

Discussion 9 - Circuits

Problem 1. The circuit shown in Figure 1 contains two batteries, each with an emf and an internal resistance, and two resistors.

- Find the current in the circuit (magnitude and direction)
- Find the terminal voltage V_{ab} of the 16.0 V battery.
- Find the potential difference V_{ac} of the point a with respect to the point c.

Problem 2. Consider the circuit shown in Figure 2. The battery has emf \mathcal{E} and negligible internal resistance. After the capacitors have attained their final charges, the charge on C_1 is Q_1 .

- What is the final charge on C_2 ?
- What is the resistance R_1 in terms of R_2 , C_1 , Q_1 , and \mathcal{E} ?

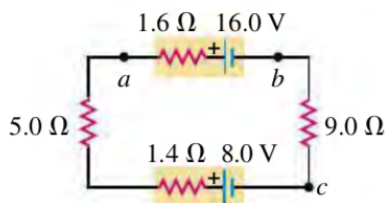


Figure 1: Problem 1

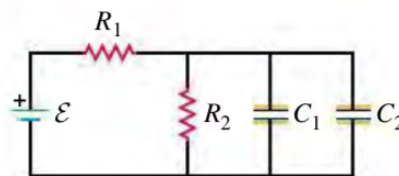


Figure 2: Problem 2

Problem 3. In the circuit shown in Figure 3 the batteries have negligible internal resistance and the meters are both idealized. With the switch S open, the voltmeter reads 15.0 V.

- Find the emf \mathcal{E} of the battery.
- What will the ammeter read when the switch is closed?

Problem 4. In the circuit shown in Figure 4 both capacitors are initially charged to V_0 .

- How long after closing the switch S will the potential across each capacitor be reduced to $V = FV_0$ where $F < 1$?
- What will be the current at that time?

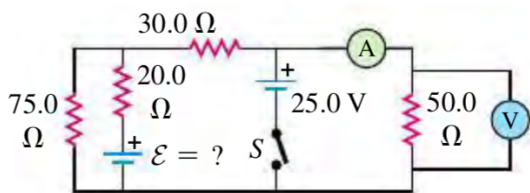


Figure 3: Problem 3

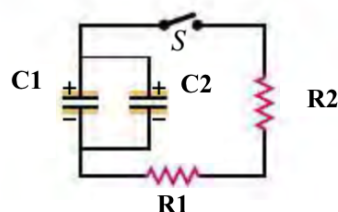


Figure 4: Problem 4