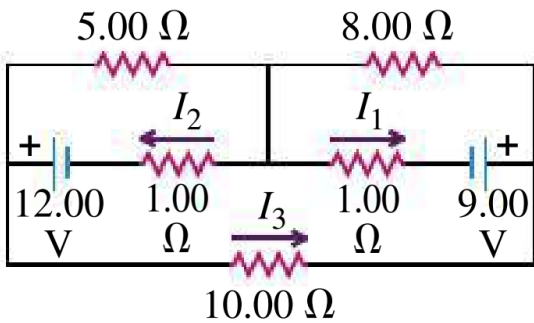



**26.59** • Calculate the three currents  $I_1$ ,  $I_2$ , and  $I_3$  indicated in the circuit diagram shown in **Fig. P26.59**.

Figure **P26.59**




**26.61** • Find the current through each of the three resistors of the circuit shown in **Fig. P26.61**. The emf sources have negligible internal resistance.

Figure **P26.61**

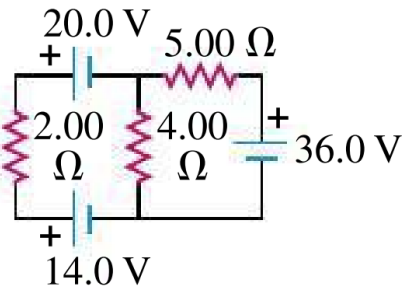

**26.62** • (a) Find the current through the battery and each resistor in the circuit shown in **Fig. P26.62**. (b) What is the equivalent resistance of the resistor network?


Figure **P26.62**

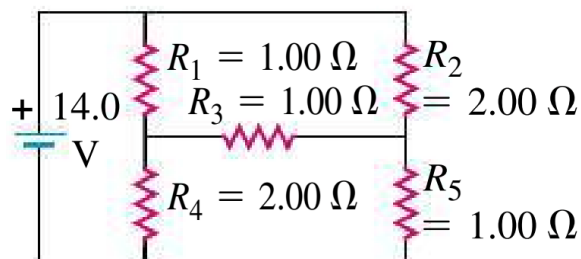

**26.63** •• Consider the circuit shown in **Fig. P26.63**.


(a) What must the emf  $\mathcal{E}$  of the battery be in order for a current of 2.00 A to flow through the 5.00-V battery as shown? Is the polarity of the battery correct as shown? (b) How long does it take for 60.0 J of thermal energy to be produced in the 10.0- $\Omega$  resistor?

Figure **P26.63**

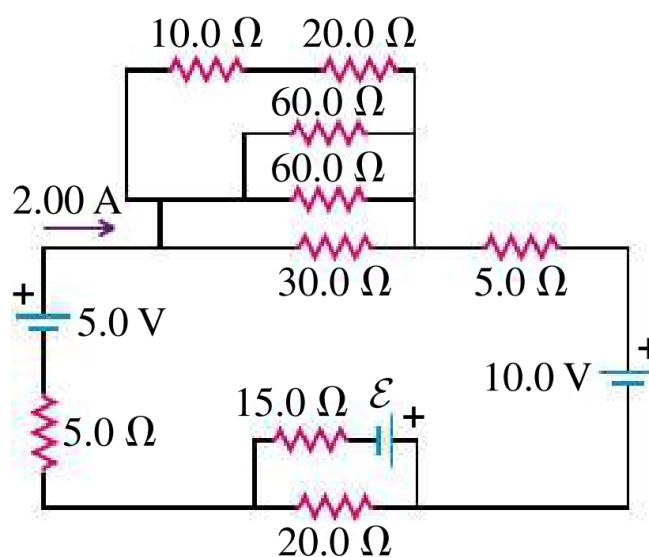


**26.47 •• CP** In the circuit shown in **Fig. E26.47** each capacitor initially has a charge of magnitude  $3.50 \text{ nC}$  on its plates. After the switch  $S$  is closed, what will be the current in the circuit at the instant that the capacitors have lost 80.0% of their initial stored energy?

Figure **E26.47**

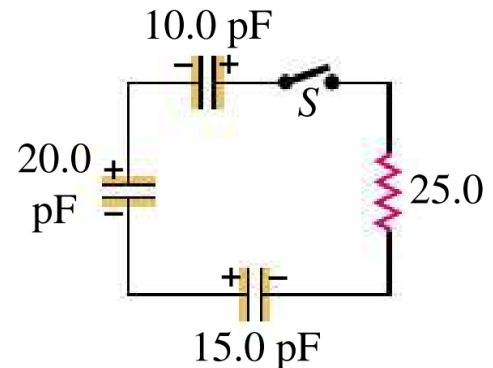


**26.49 •** In the circuit in **Fig. E26.49** the capacitors are initially uncharged, the battery has no internal resistance, and the ammeter is idealized. Find the ammeter reading (a) just after the switch  $S$  is closed and (b) after  $S$  has been closed for a very long time.

Figure **E26.49**

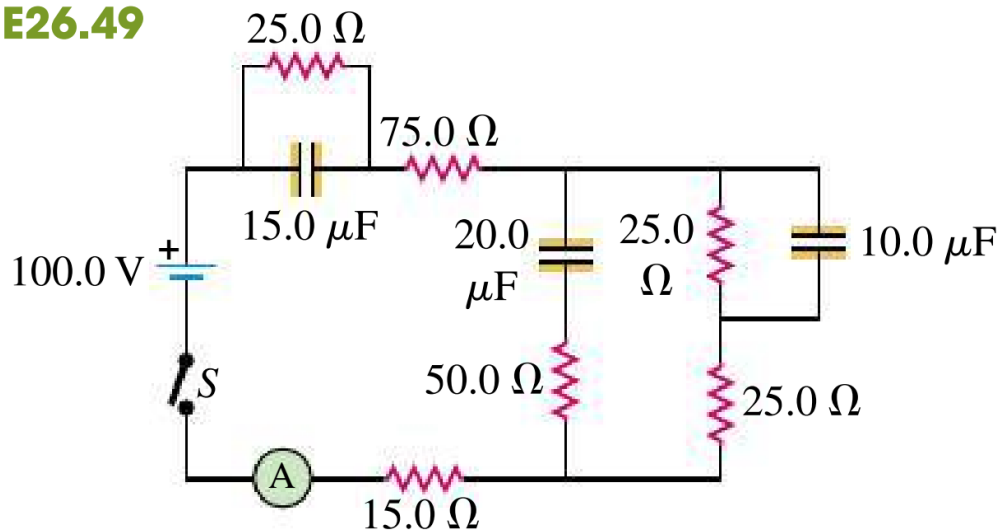

**26.70 •** The capacitor in **Fig. P26.70** is initially uncharged. The switch  $S$  is closed at  $t = 0$ . (a) Immediately after the switch is closed, what is the current through each resistor? (b) What is the final charge on the capacitor?

Figure **P26.70**

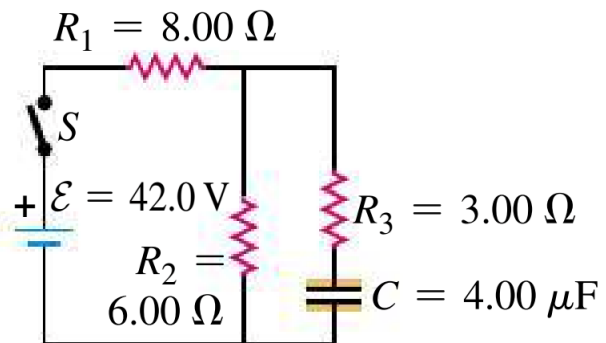

**26.75 •** (See Problem 26.67.) (a) What is the potential of point  $a$  with respect to point  $b$  in **Fig. P26.75** when the switch  $S$  is open? (b) Which point,  $a$  or  $b$ , is at the higher potential? (c) What is the final potential of point  $b$  with respect to ground when  $S$  is closed? (d) How much does the charge on each capacitor change when  $S$  is closed?

Figure **P26.75**

