

# DC Circuits Kudu Graded Homework Solutions

## Question 1

All resistors in parallel will yield the smallest equivalent resistance.

Series:  $R_{eq} = R_1 + R_2 + R_3 \dots$


Adding resistors in series always increases equivalent resistance.

Parallel:  $R_{eq} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}}$


Adding resistors in parallel increases the denominator, thus decreasing the resistance.
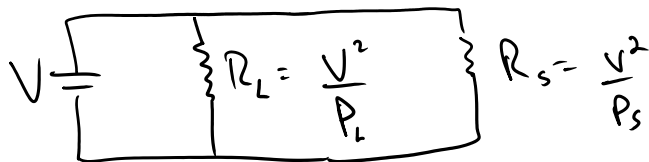
## Question 2

Given  $P_L$ ,  $P_S$  when connected in parallel. Use:  $P = \frac{V^2}{R} \rightarrow R_i = \frac{V^2}{P_i}$




In Series:  $R_L$

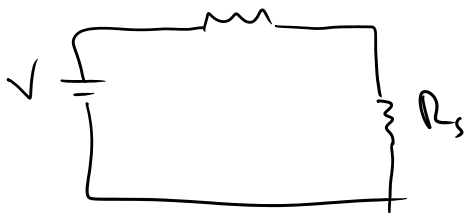

$$P = \frac{V^2}{R_{eq}} = \frac{V^2}{R_L + R_S} = \frac{V^2}{\frac{V^2}{P_S} + \frac{V^2}{P_L}}$$

$$P = (P_S^{-1} + P_L^{-1})^{-1}$$

## Question 3

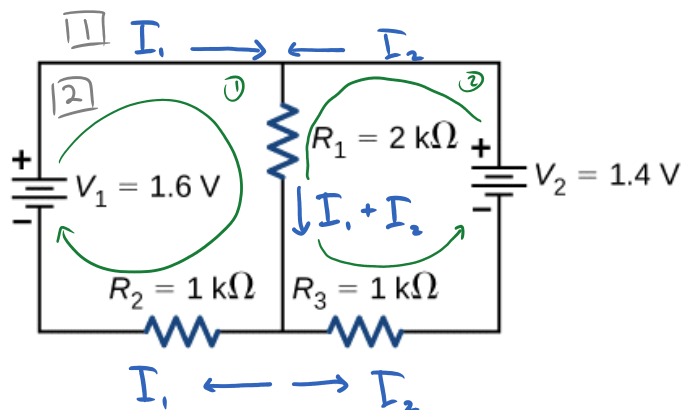

1 We don't know the direction of  $I$ 's. We guess. If solving produces negative  $I$ , then we know direction is flipped. Guessing:

2 Choose loops. Have 2 unknowns, need 2 equations. Will use 2 loops:

Loop 1:  $V_1 - (I_1 + I_2)R_1 - I_1R_2 = 0 \rightarrow I_1 = \frac{V_1 - I_2R_1}{R_1 + R_2}$


Loop 2:  $V_2 - (I_1 + I_2)R_1 - I_2R_3 = 0$   
 Use above sol.  $= R_2$

Algebra ...

$$I_2 = \frac{V_2(R_1 + R_2) - R_1V_1}{R_2(2R_1 + R_2)} = 0.2 \text{ mA} \rightarrow I_1 = \frac{V_1 - I_2R_1}{R_1 + R_2} = 0.4 \text{ mA}$$

$$I_1 + I_2 = \boxed{0.6 \text{ mA}}$$

#### Question 4

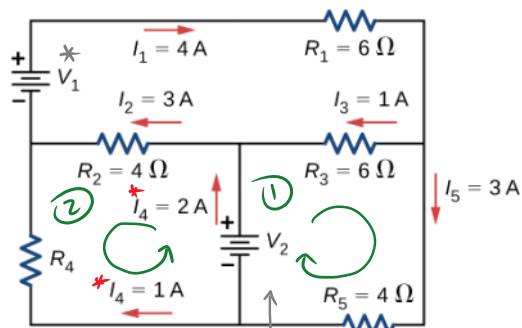

Using this loop to find  $V_2$

\*  $V_1$  unknown. Avoiding.

①  $V_2 + I_3R_3 - I_5R_5 = 0 \rightarrow V_2 = 6V$   
 All known


$$V_2 = I_5R_5 - I_3R_3 = 6V$$

②  $V_2 - I_2R_2 + I_4R_4 = 0$   
 All known

$$R_4 = (I_2R_2 - V_2) / I_4 = \boxed{6 \Omega}$$

#### Question 5

Use:  $P = I^2R$

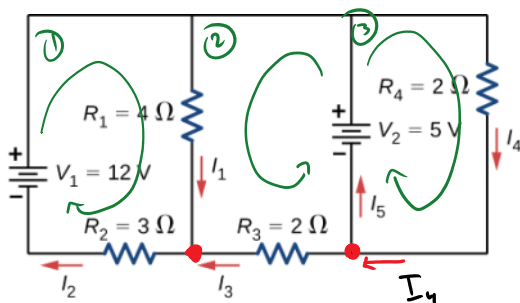

#### Junction Rule

- $I_1 + I_3 = I_2$
- $I_3 + I_5 = I_4$

3 unknowns left. Need 3 more equations.  
 Use loop rule

## Loop Rule

$$1. V_1 - I_1 R_1 - \overset{= I_2}{(I_1 + I_3)} R_2 = 0 \rightarrow I_1 = \frac{V_1 - I_3 R_2}{R_1 + R_2}$$

$$2. V_2 - I_1 R_1 + I_3 R_3 = 0$$

$$I_3 = \frac{V_2(R_1 + R_2) - V_1 R_1}{R_1(R_2 + R_3) + R_2 R_3} = 0.5 \text{ A}$$

$$I_1 = \frac{V_1 R_3 + V_2 R_2}{R_1(R_2 + R_3) + R_2 R_3} = 1.5 \text{ A}$$

$$I_2 = I_1 + I_3 = 2 \text{ A}$$

$$3. V_2 - I_4 R_4 = 0 \rightarrow I_4 = \frac{V_2}{R_4} = 2.5 \text{ A}$$

$$I_5 = I_4 - I_3 = 2 \text{ A}$$

$$P = I_1^2 R_1 + I_2^2 R_2 + I_3^2 R_3 + I_4^2 R_4 = \boxed{34 \text{ W}}$$

## Question 6



Alkaline cells:  $V_1$   
Carbon-zinc:  $V_2$

Note: the battery makeup is irrelevant.

$$3(V_1 - I r_1) + V_2 - I r_2 - I R = 0$$

$$3V_1 + V_2 = 3I r_1 + I r_2 + I R$$

$$= I(3r_1 + r_2 + R)$$

$$I = \frac{3V_1 + V_2}{3r_1 + r_2 + R}$$

### Question 7

$$\tau = RC$$


$$\text{Range: } C(R_1, R_2) = (2, 15),$$

$$(R_1, R_2) = \frac{1}{0.5 \mu F} (2, 15),$$

$$= \boxed{(4, 30) M\Omega}$$
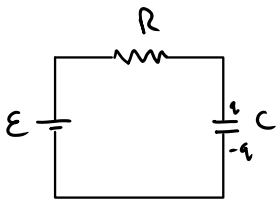
### Question 8

This problem doesn't state whether the capacitor is initially charged or discharged. But it does not matter, because the current equation for both cases is the same.



$$I = I_0 e^{-t/\tau} = \frac{\varepsilon}{R} e^{-t/\tau}$$

$$\tau = RC$$

$$I(\tau) = \frac{\varepsilon}{R} e^{-1}$$

### Question 9

$$\text{Need: } \tau < 100 \mu s$$


$$\tau = RC$$

$$\text{Given: } R = 1 k\Omega$$

$$C < \frac{100 \mu s}{R} \rightarrow \text{Max } C = \frac{100 \mu s}{1 k\Omega} = \boxed{100 \mu F}$$
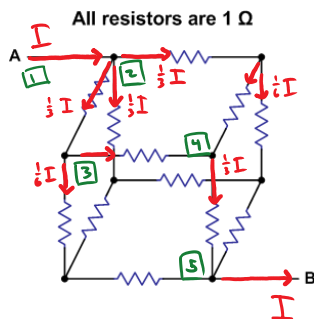
### Question 10

This requires the Kirchhoff's Junction Rule and Ohm's Law to solve.



- [1] If points A and B were connected to the terminals of a battery, then the current  $I$  out of the battery at point A MUST be the current into the battery at point B. This allows us to write:

$$V_A - V_B = I R_{eq}$$

- [2] Because all resistors are the same, the current will split evenly at the first junction.

- [3] Because all resistors are the same, the current will split evenly at this junction.

- [4]  $\frac{1}{6}I$  and  $\frac{1}{6}I$  combine and produce current out  $\frac{1}{3}I$ .

- [5]  $\frac{1}{3}I + \frac{1}{3}I + \frac{1}{3}I$  combine to produce current out  $I$ .

$$\text{Any path we follow from A to B will yield: } V_A - V_B = \frac{1}{3}IR + \frac{1}{6}IR + \frac{1}{3}IR = \frac{5}{6}IR = IR_{eq}$$

$$\Rightarrow \boxed{R_{eq} = \frac{5}{6}R}$$